

Lab 7: The MOS Differential Pair

Pranavi Boyalakuntla

Skye Ozga

Experiment 1: Differential Pair Current-Voltage Characteristics

In this experiment, we constructed an nMOS differential pair with a bias voltage that set the bias current right at threshold (0.6 V) and a V_2 far enough away from the power supply rail such that the bias transistor is saturated. We measured I_1 and I_2 and the common-source node voltages as a function of V_1 (swept from slightly below V_2 to slightly above V_2). We also repeated this procedure for two more values of V_2 that satisfied the criteria established above.

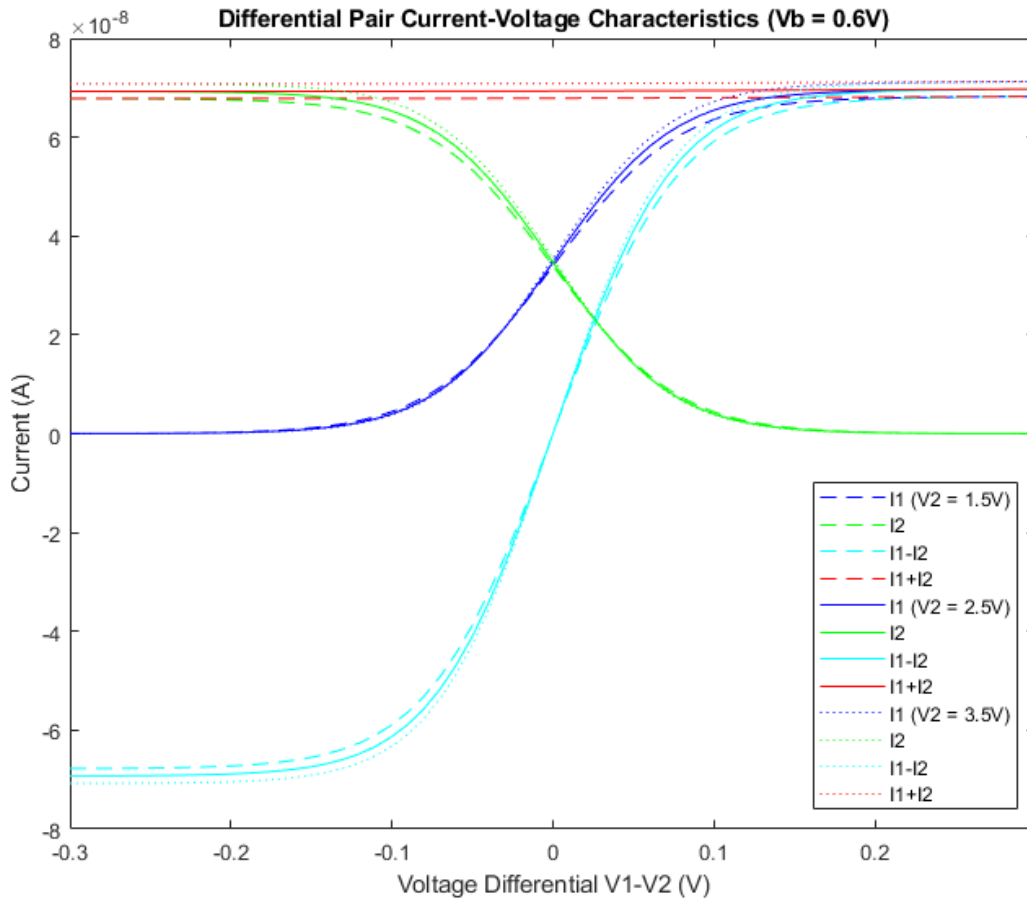


Figure 1: The current outputs as a function of the voltage differential ($V_1 - V_2$) for several values of V_2 and a swept V_1 with the bias current below threshold.

Referring to figure 1, the current voltage characteristics do not change significantly with different values of V_2 . In fact, they stick pretty closely together. As expected, V_2 values don't impact the output current proportionally.

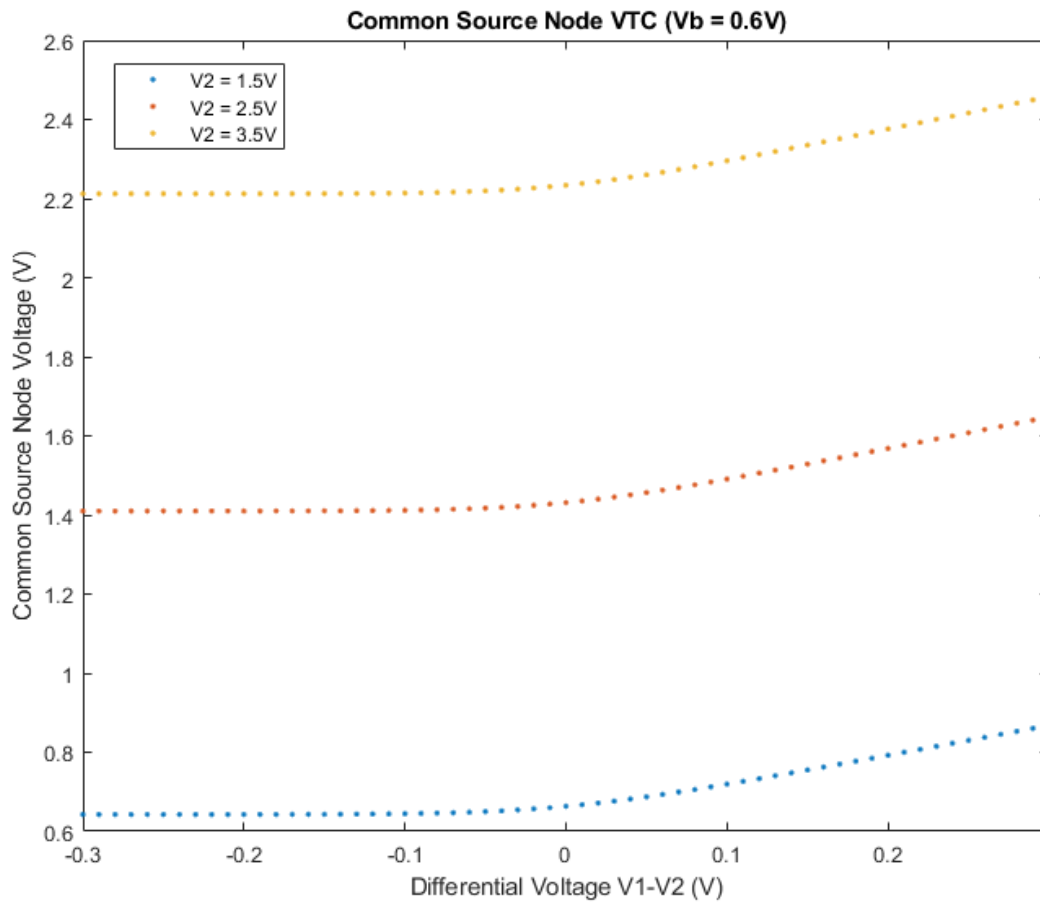


Figure 2: The common-source node voltage as a function of the V_{dm} for 3 separate values of V_2 with the bias current below threshold.

The slope of the common source node voltage increases once the differential mode voltage is positive. This trend is followed equally at all three V_2 values.

Table 1

<u>Aa</u> V_2 Value	<u>≡</u> Differential-Mode Transconductance Gain (Mhos)
<u>1.5V</u>	8.565e-7
<u>2.5V</u>	9.121e-7
<u>3.5V</u>	9.521e-7

At the three V_2 values, the differential-mode transconductance gain does increase slightly with V_2 , but, as expected, it doesn't change it even remotely proportionally to how much V_2 is changing.

For the latter half of this experiment, we set the bias voltage (1.0 V) such that the bias current is above threshold. We used a value of V2 that is far enough from the power supply rail to keep the bias transistor saturated (1.5 V, 2.5 V, 3.5 V).

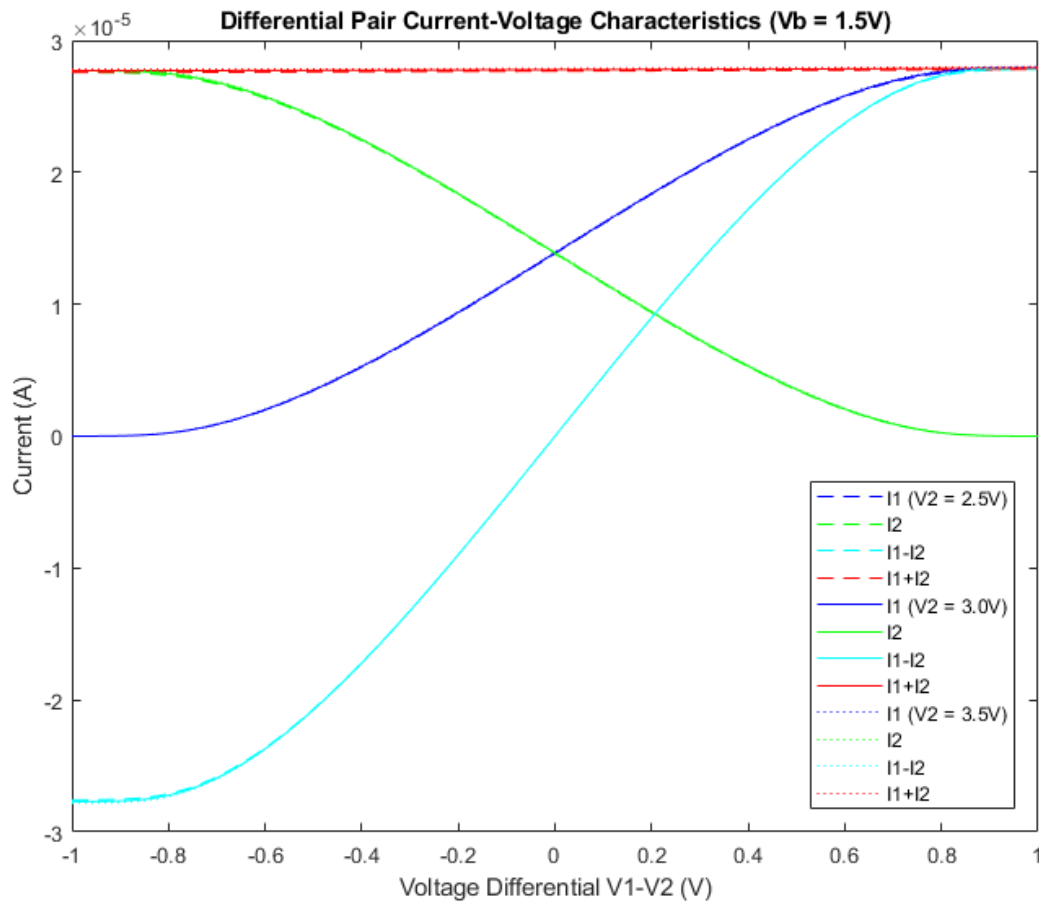


Figure 3: The current outputs as a function of the voltage differential ($V_1 - V_2$) for several values of V_2 and a swept V_1 with the bias currents above threshold.

Table 2

<u>Aa</u> V2 Value	<u>≡</u> Differential-Mode Transconductance Gain (Mhos)
<u>1.5 V</u>	4.549e-5
<u>2.5 V</u>	4.550e-5
<u>3.5 V</u>	4.545e-5

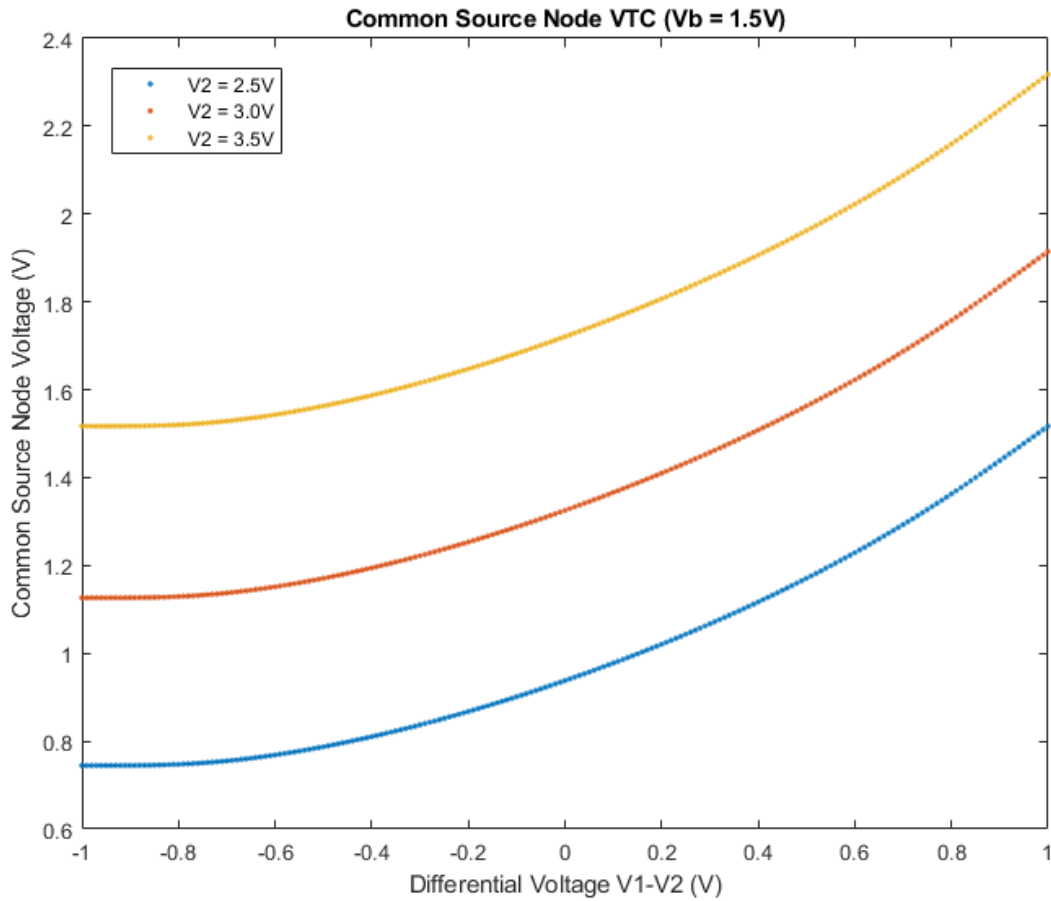


Figure 4: The common-source node voltage as a function of the V_{dm} for 3 separate values of V_2 with the bias current above threshold.

The current-voltage characteristic plots for the bias currents below and above threshold are very similar. It seems that V_2 affects the differential-mode transconductance gain in a similar way at bias currents above and at threshold. In addition, the behavior between are similar in both.

The common source node voltage transfer characteristics were similar at bias currents above and at threshold. However, at the bias current just below threshold, there was a clear change in the behavior at the differential mode voltage 0. At the bias current significantly above threshold, the common source node voltage plot follows a much smoother and exponential curve.

Lastly, although the trends followed are similar, the range of V_1 s needed to sweep through to capture all of the trends was larger. This is because the transition range to saturate is much larger at strong inversion.

